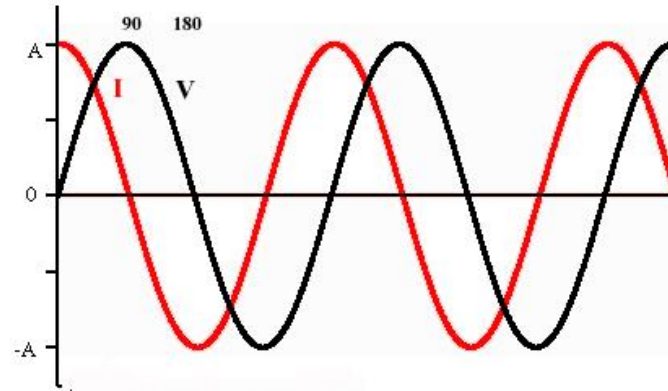


Module 4 Theory

- IRTS Region 4

Capacitive Reactance




- When a.c. is applied to a capacitor it will charge it, first in one direction, then the other; max. current flows when the voltage is changing most rapidly, least as voltage peaks
- The current **leads** the voltage by 90°

Capacitive Reactance

- The ratio of voltage to current is the reactance (X_C) measured on Ohms (Ω)
- $X_C = V / I$; $I = V / X_C$; $V = IX_C$
V, I are rms values
- $X_C = \frac{1}{(2\pi f C)}$ Reactance decreases as frequency increases

Inductive Reactance

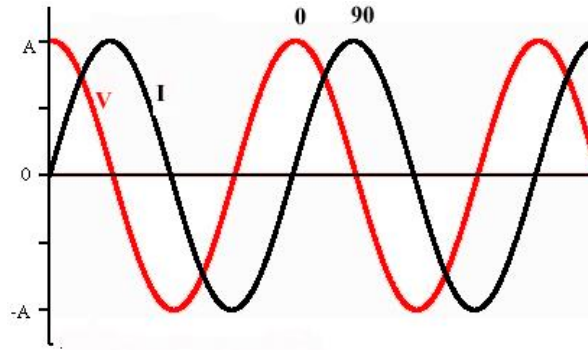

- If an a.c. voltage is applied to an inductor the reverse voltage (**back emf**) generated causes the current to **lag** the voltage by 90°
- The ratio of voltage to current is the reactance (X_L) measured on Ohms (Ω)
- $X_L = V / I$; $I = V / X_L$; $V = I X_L$
[V, I are rms values]
- $X_L = 2\pi f L$ Reactance increases with frequency

Q-factor

- An ideal inductor has no resistance to d.c. In practice there will be losses due to wire resistance, core losses (due to induced currents in conductive cores) and **skin effect**, whereby as frequency increases a.c. tends to flow only on the conductor surface
- The ratio of reactance to resistive losses for either a capacitor or inductor is called the **Q-factor** $Q = X / R$ [Q has no units]

Shielding & Earthing

- Equipment should be adequately shielded, generally in an earthed metal enclosure.
- This prevents radiation leaving or entering the device
- A separate RF earth will prevent signals flowing on the mains (safety) earth; it will also reduce noise pick-up by the amateur station
- This separate earth should consist of several earth rods, connected by thick wire or braid

Screening

- Screening is used to prevent coupling between circuits.
- **Magnetic screens:**
 - **A soft magnetic material is introduced to concentrate the flux lines leaving the field weaker elsewhere. Materials such as Mu-metal may be used for this.**
- **Electrostatic screening:**
 - **Is when a conductor is surrounded completely by another conductor which has the same potential along its whole length - sometimes called a Faraday Cage**
- Take care that screens are not too close and unduly influence circuitry they are meant to protect.


Electric field

- An **electric field** is the force resulting from electric charges
- **Field strength** is measured in **volts/meter**
- The effects of spurious electric fields can be reduced by screening equipment with earthed conductive material

Magnetic Field

- Every current-carrying conductor has a **magnetic field** around it caused by the current
- Unwanted effects can be reduced by shielding with a magnetic shielding alloy called Mumetal

Electromagnetic Field

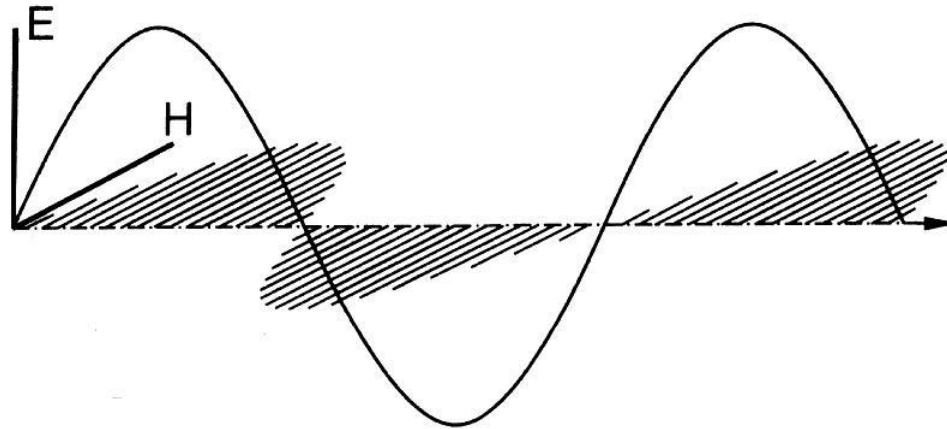

- A **radio wave** is an **electromagnetic wave**, consisting of **electric (E)** and **magnetic (H)** fields at right angles to each other, both at right angles to the direction of travel
- The E-field determines **polarisation** and **field strength** (example is vertically polarised)

Propagation Velocity


- The speed at which the wave travels (**propagation velocity**) depends on the medium in which it is travelling
- In free space it travels at the speed of light (300×10^6 m/s). In air velocity is slightly less
- *velocity = frequency \times wavelength*
- $v = f \times \lambda$; λ (meters) = $300 / f$ (MHz)
- 6 MHz is a wavelength of 50 meters

Power Supplies

- **Mains On/Off switch** should be double pole isolating both the live and the neutral
- A mains fuse of appropriate value should be fitted in the **live lead only** on the equipment side of the mains switch
- A fuse or fuses of appropriate value should be fitted on the output/s of the power supply

Mains Plugs Fitting

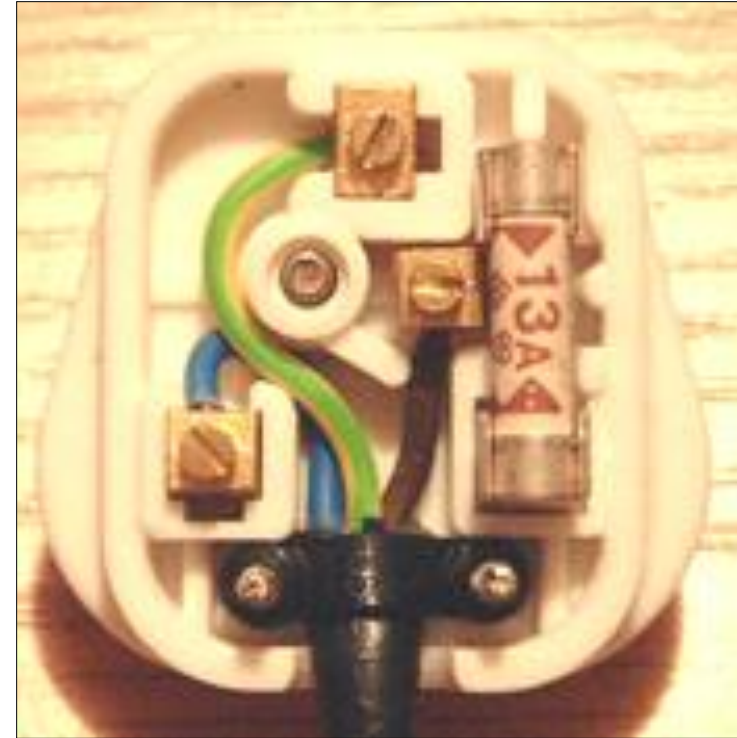- Flex Colours:-
- Live=**Brown**,
- Neutral=**Blue**
- Earth=**Green / Yellow**
- Avoid whiskers, trapped wires, and ensure that Cord Grips are secure, but don't pierce the insulation.
- Fuses are to protect the equipment and you.
- **ALWAYS FIT THE RIGHT FUSE FOR THE EQUIPMENT**



Power Supplies


- Micro switches should be installed so that high voltage supplies for valve power amplifier stages are **automatically disconnected** when the cover is removed
- In high voltage power supplies a **bleeder resistor** should be connected across each smoothing capacitor to allow them to discharge after the power is switched off

Power Supplies

- Do not rely on bleeder resistors. They can go open circuit. Use a shorting stick to ensure high voltage smoothing capacitors are discharged
- **Switch off before replacing fuses**

Power Supplies - 1


Half Wave Rectification

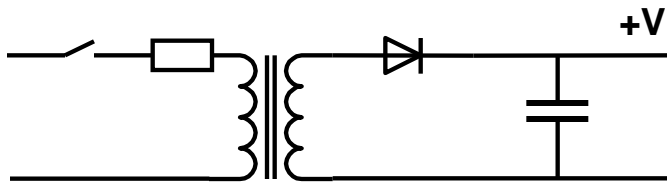

Best suited to low current applications

- High Ripple Current and Low Efficiency.
- Diode PIV = $2.8 \cdot V_{ac}$

Full Wave Rectification

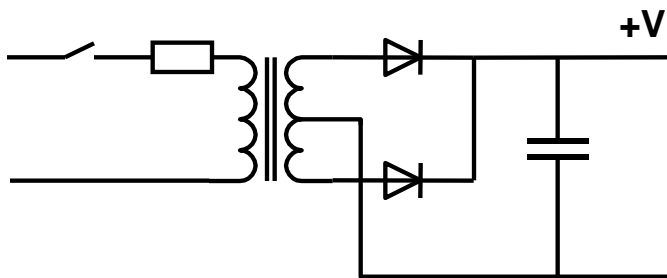


Circuit also known as Bi-Phase rectification. Each diode conducts on one half cycle. DC component of load flows through the secondary in such a direction to cancel magnetising current.

- Diode PIV = $2.8 \cdot V_{ac}$

Power Supplies - 2

Bridge Rectification

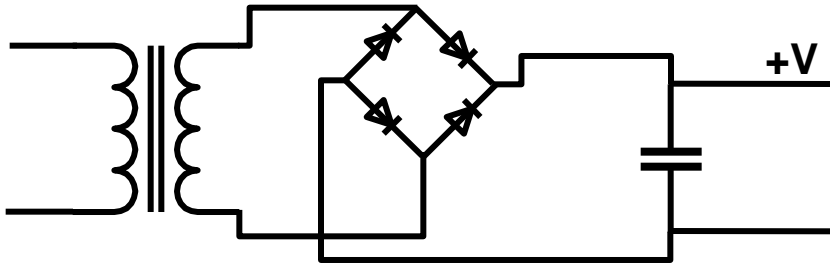


Preferred for high voltage, and does not need a centre-tapped transformer.

During each half cycle of the input voltage two of the diodes are conducting.


- PIV is half per diode.
- Diode PIV = $1.4 \cdot V_{ac}$

Smoothing Circuits - 1

Simple Capacitor Filter

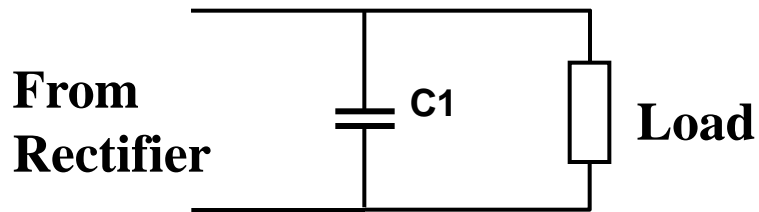


Capacitor Input Filter

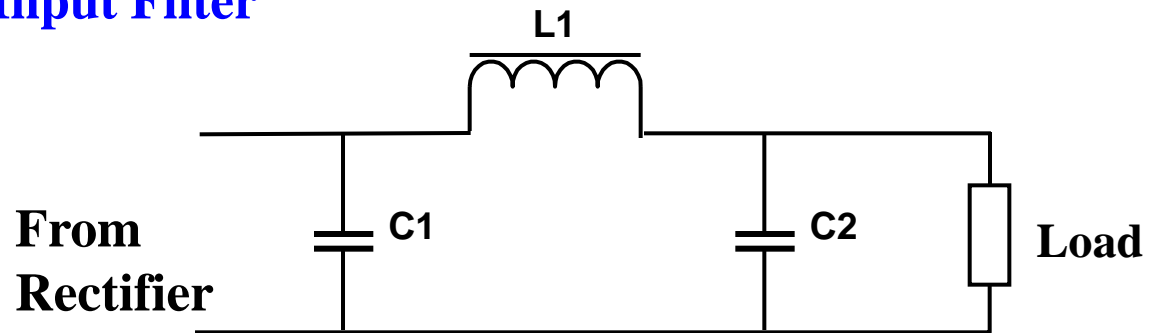


Smoothing Circuits - 2

Choke Input Filter

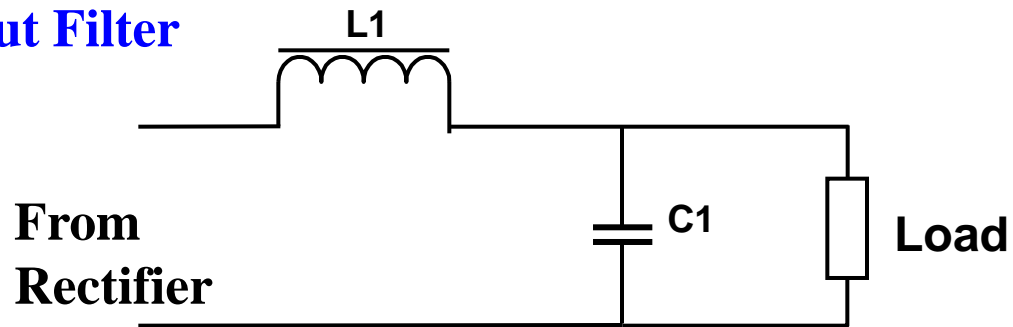


Resistance Capacitance Filter

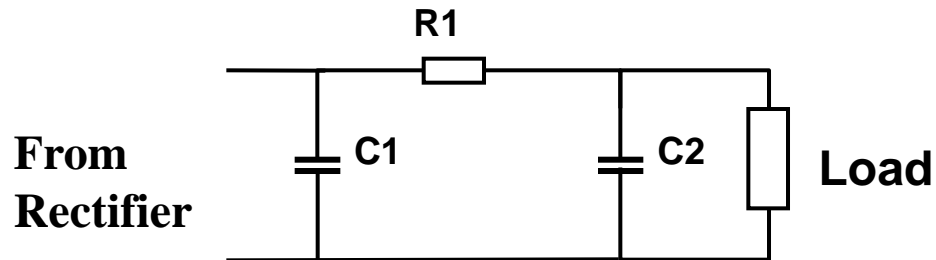


Stabilising Circuits

Zener Diode

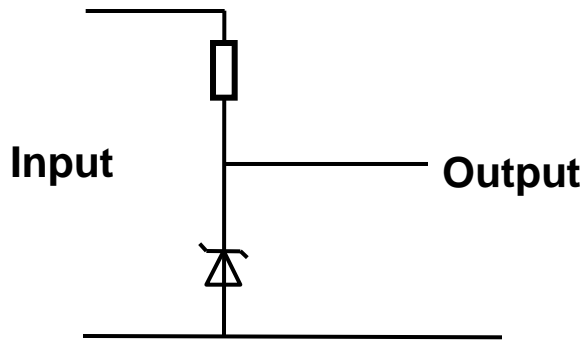

Pass Transistor

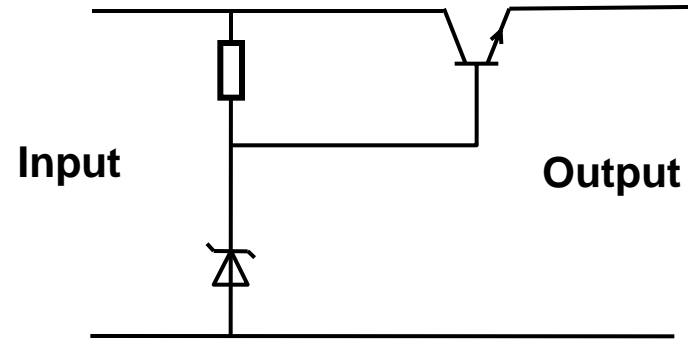

IC Regulator

